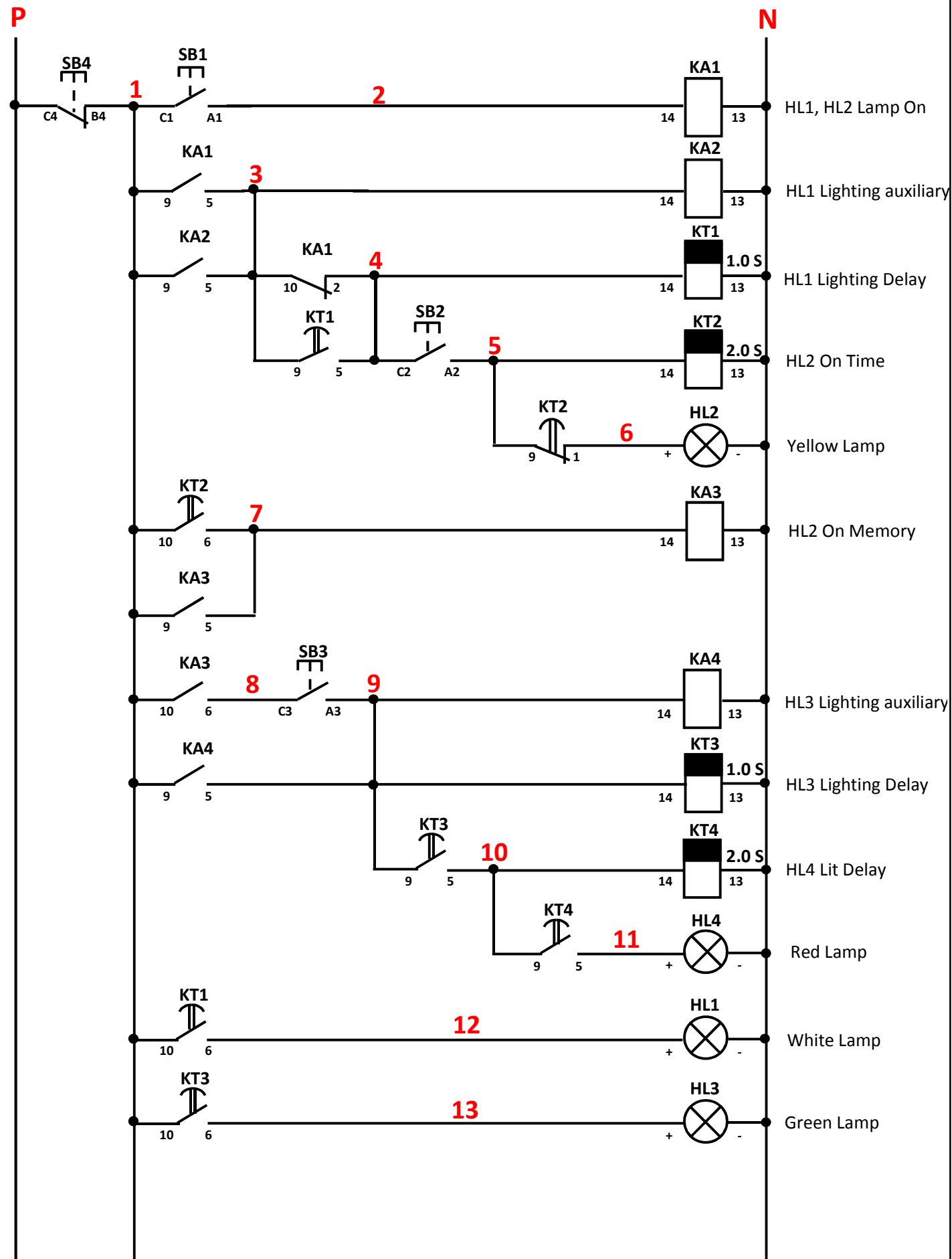


Control circuit Relay TMC_Ex_03



- ①After [KT1] time up by [SB1] ON→OFF, [HL1] lights up.
- ② [HL2] lights up while [SB2] is ON, and turns off when [KT2] time is up.
- ③When [SB3] is ON, [HL3] lights up after [KT3] time up, and [HL4] lights up after [KT4] time up.
- ④Reset by [SB4] ON.

≤Rising edge start, falling edge start Sequential operation>

