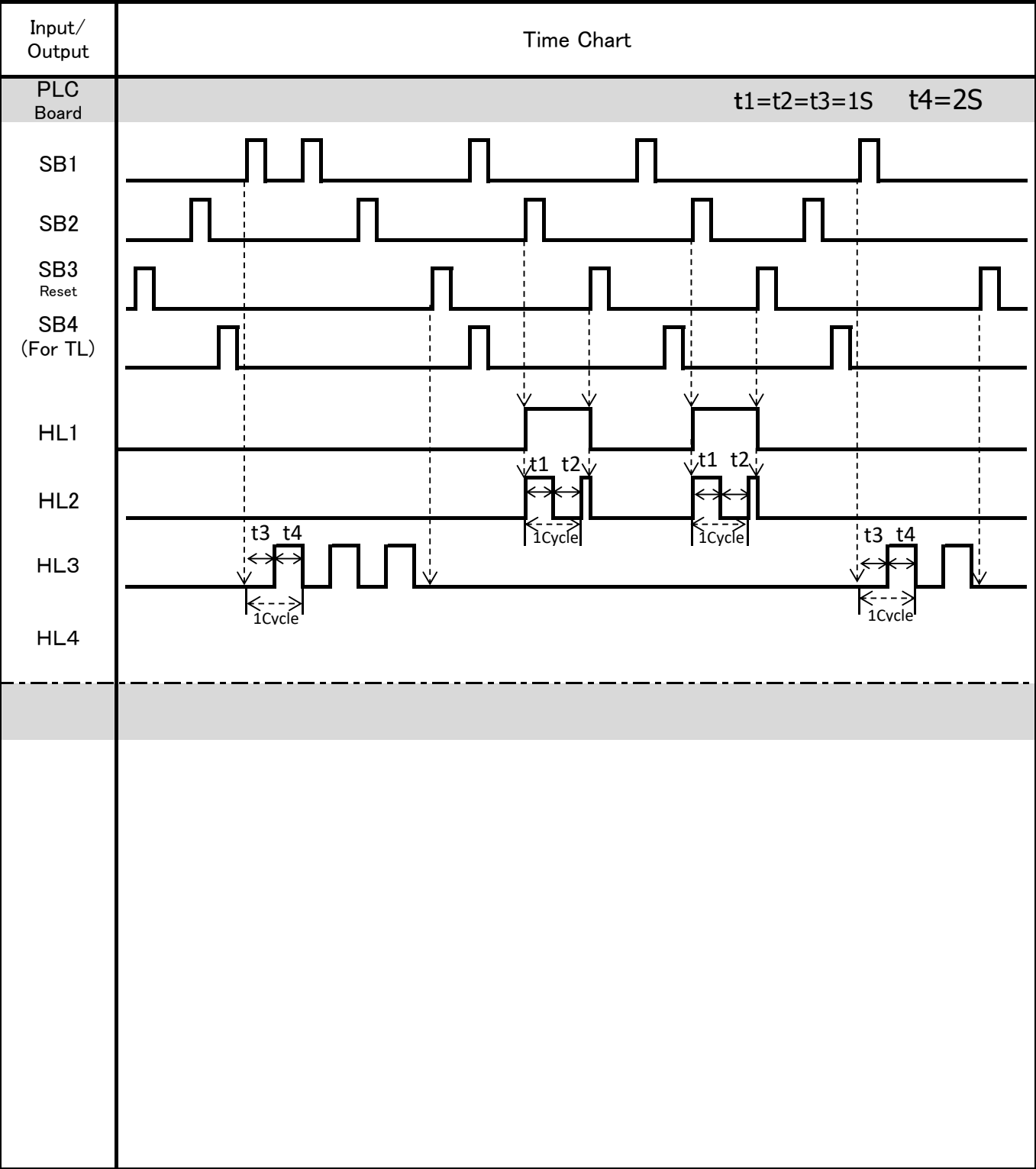



Assignment 1 PLC circuit design

Assignment content
<p>(1) Design the ladder circuit reference to the time chart.</p> <p>(2) Follow the specifications and instructions (timer settings, count timing, etc.).</p> <p>(3) Operate repeatedly (twice or more) according to the time chart.</p> <p>Design ladder circuit after the final circuit, and Do not modify the existing circuit such as the lamp check circuit.</p> <p>※ Buttons are SB1 (X000), SB2 (X001), SB3 (X002), SB4 (X003); Lamps are HL1 (Y010), HL2 (Y011), HL3 (Y012), HL4 (Y013)</p> <p>[TM] use only basic commands (application commands cannot be used), but edge detection (P) can be used.</p> <p>[TL] Basic and application commands can be used (no restrictions)</p> <p>Complete data reading and writing with FL-NET communication destinations.</p> <p>For communication settings, refer to the FL-NET communication area diagram</p>




Specification instructions (Being able to operate repeatedly. No need to consider HL other than instructions)


【HL1】Specification check cycle chart

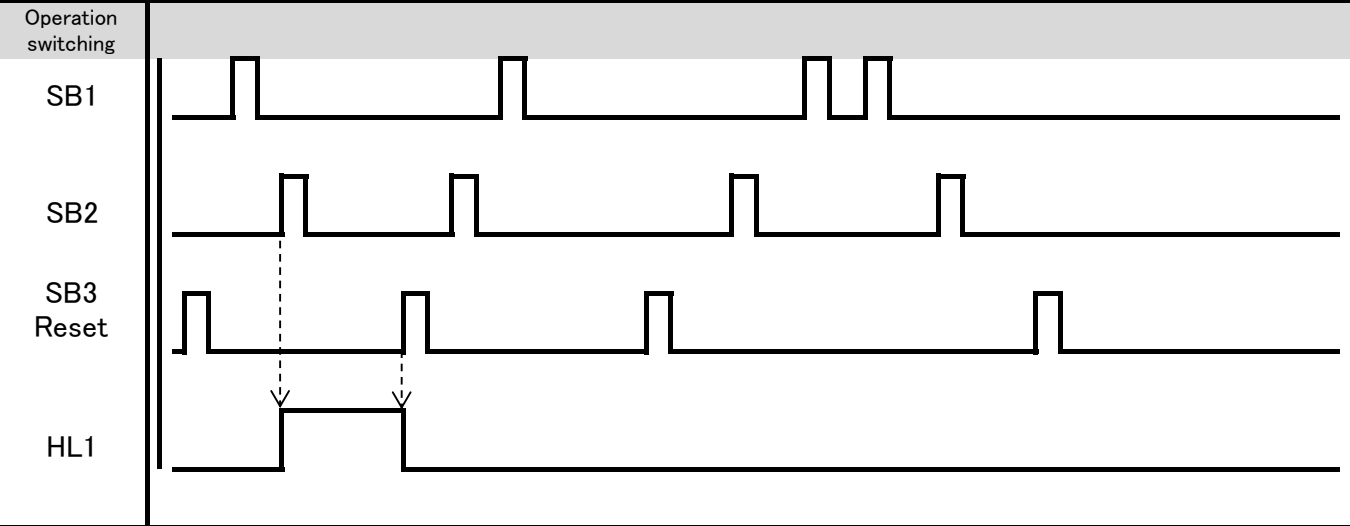

【HL2】Specification check cycle chart

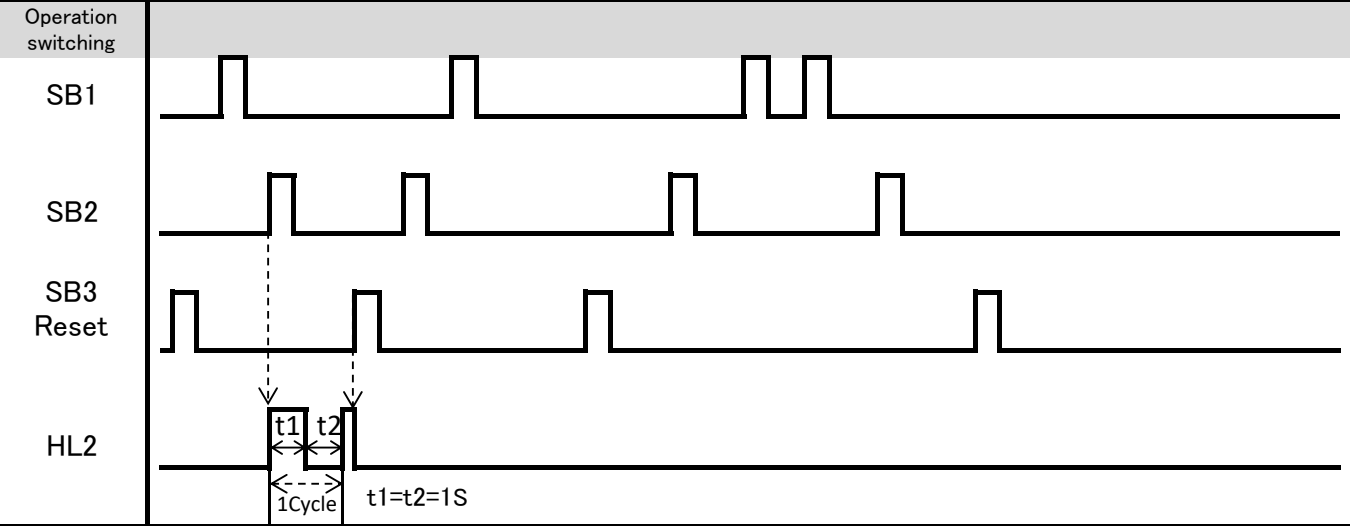

【HL3】Specification check cycle chart

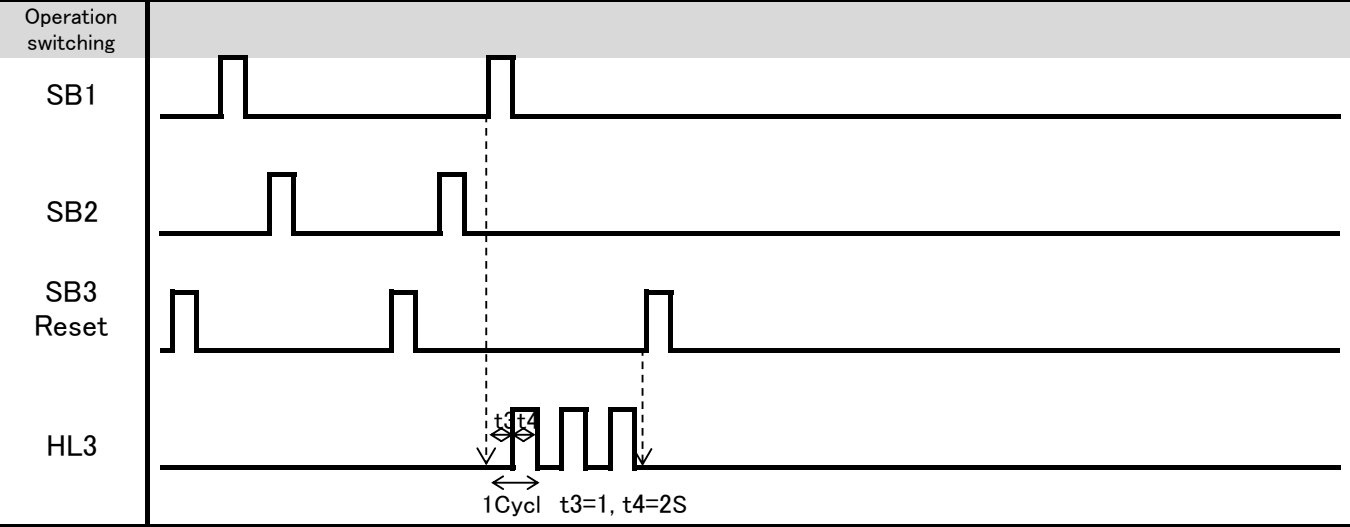

Applied problem [Multi-sequence] Specification check

peration switching	There is no relation to actions ① and ②.