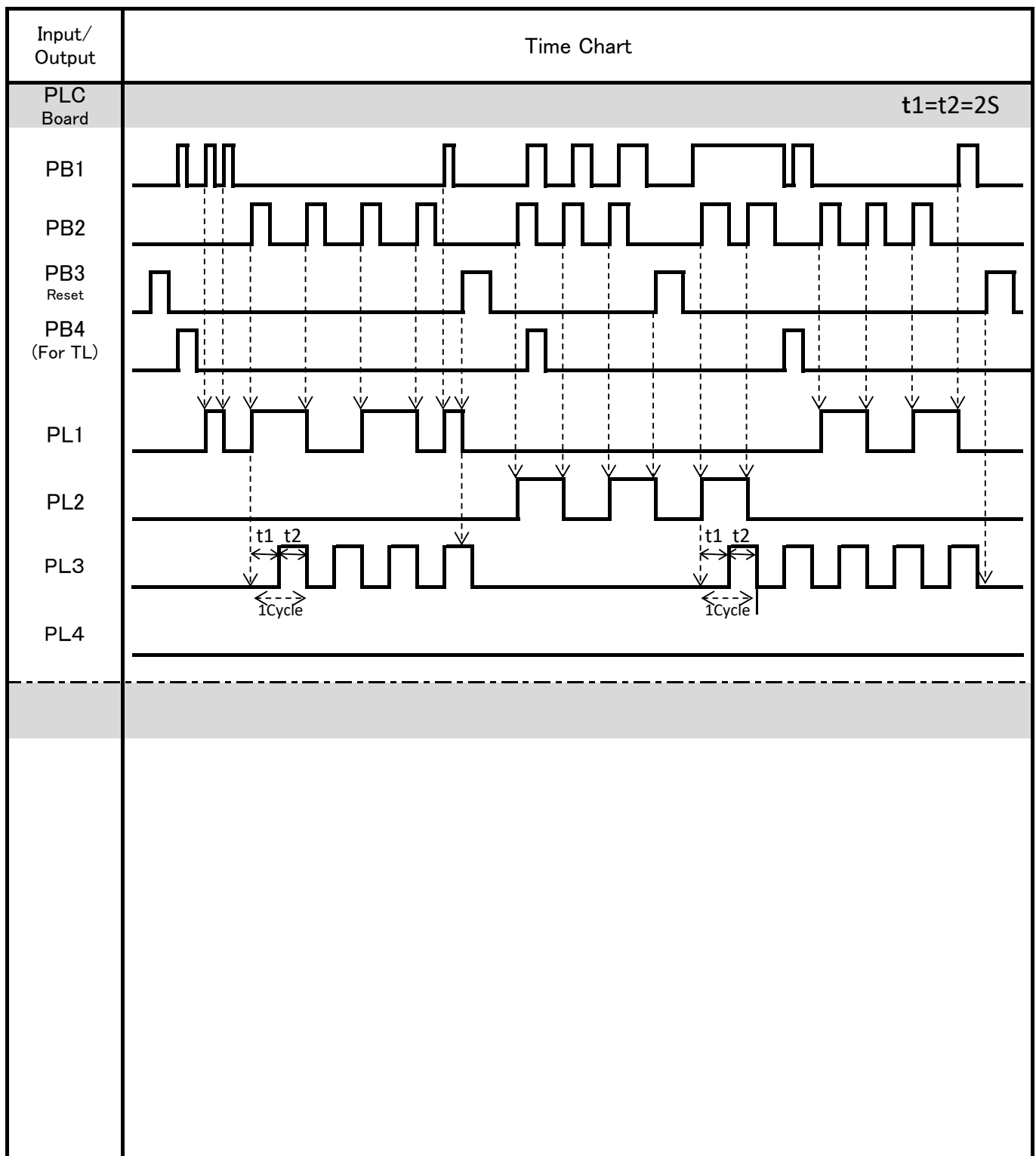


## Assignment 1 PLC circuit design


## Assignment content

- (1) Design the ladder circuit reference to the time chart.  
 (2) Follow the specifications and instructions (timer settings, count timing, etc.).  
 (3) Operate repeatedly (twice or more) according to the time chart.
- Design ladder circuit after the final circuit, and Do not modify the existing circuit such as the lamp check circuit.
- ※ Buttons are PB1 (X000), PB2 (X001), PB3 (X002), PB4 (X003); Lamps are PL1 (Y011), PL2 (Y012), PL3 (Y013), PL4 (Y014)
- [TM] use only basic commands (application commands cannot be used), but edge detection (P) can be used.
- [TL] Basic and application commands can be used (no restrictions)
- Complete data reading and writing with FL-NET communication destinations.
- For communication settings, refer to the FL-NET communication area diagram




Specification instructions (Being able to operate repeatedly. No need to consider HL other than instructions)


【PL1】Specification check cycle chart

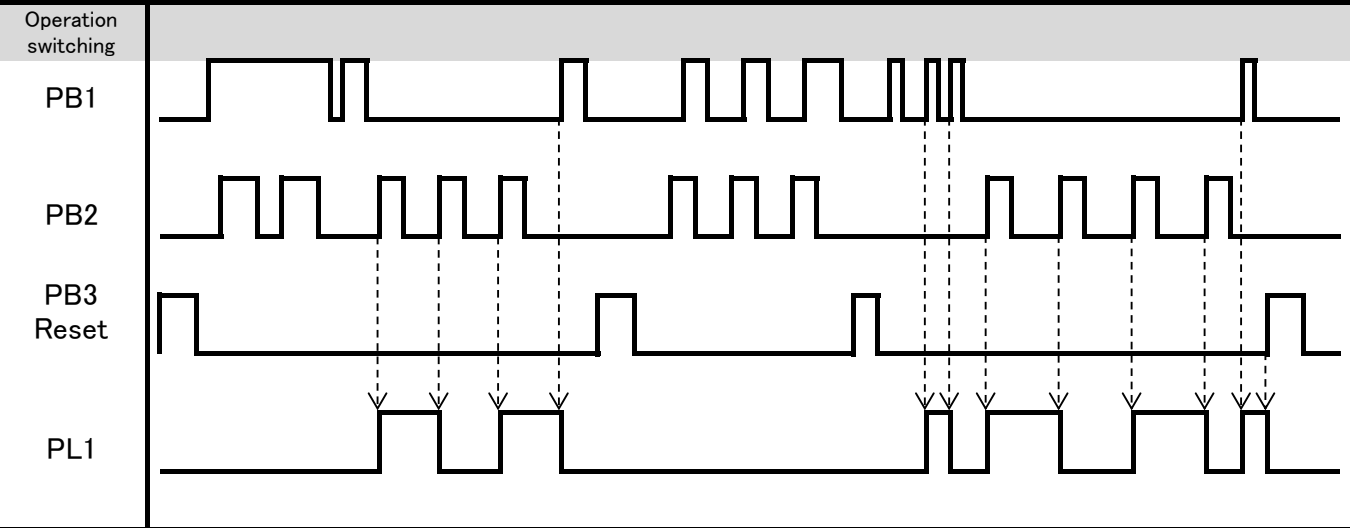

【PL2】Specification check cycle chart

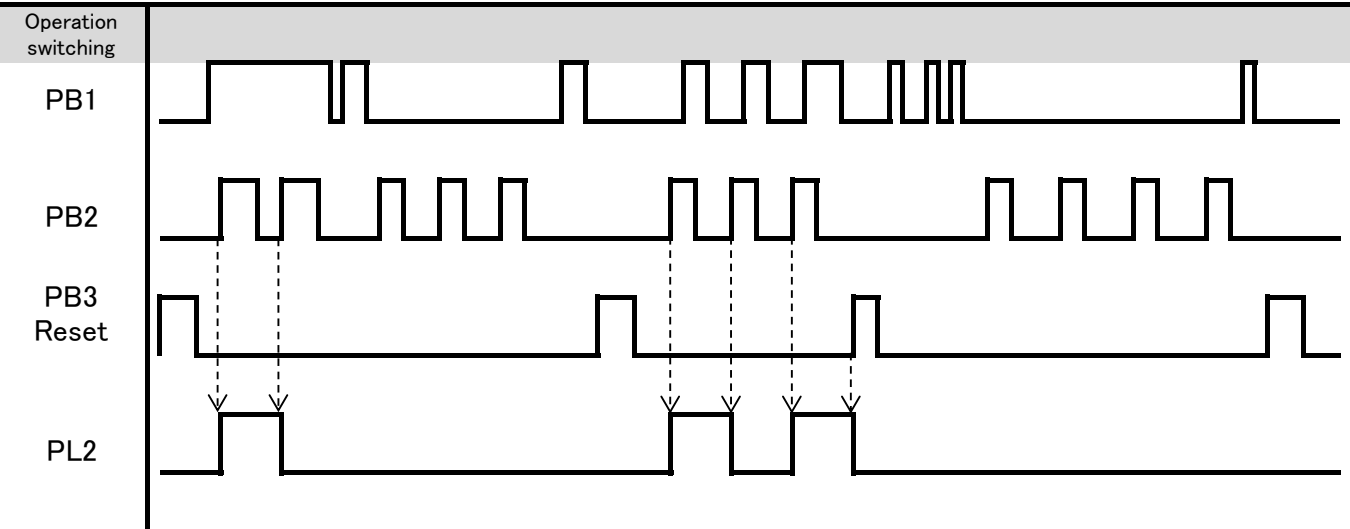

【PL3】Specification check cycle chart

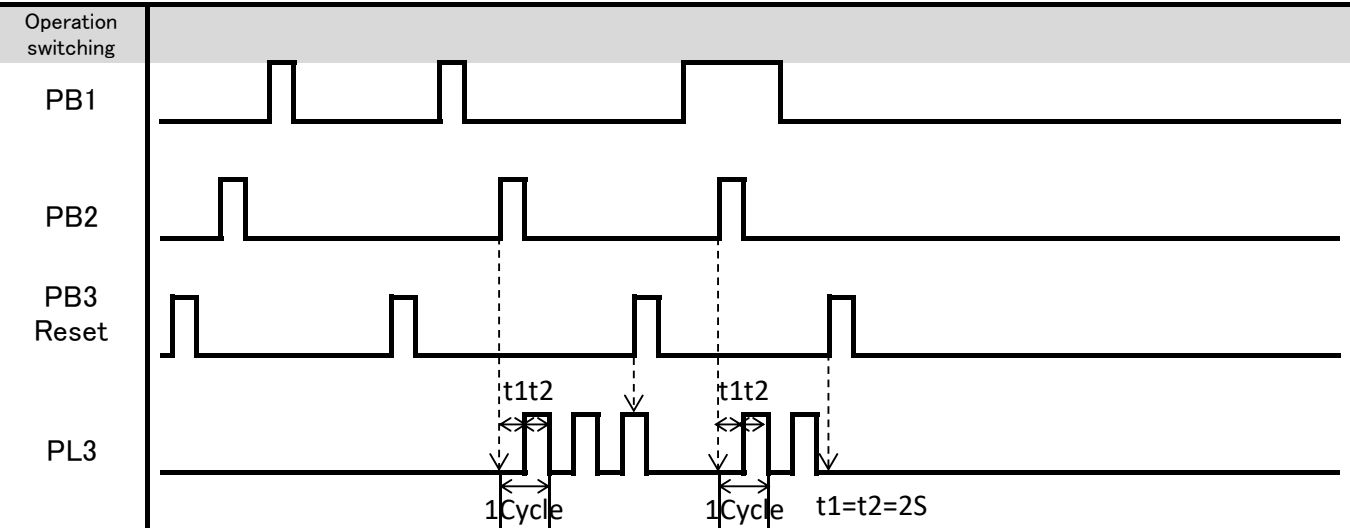

Applied problem [Multi-sequence] Specification check

peration switching	There is no relation to actions ① and ②.