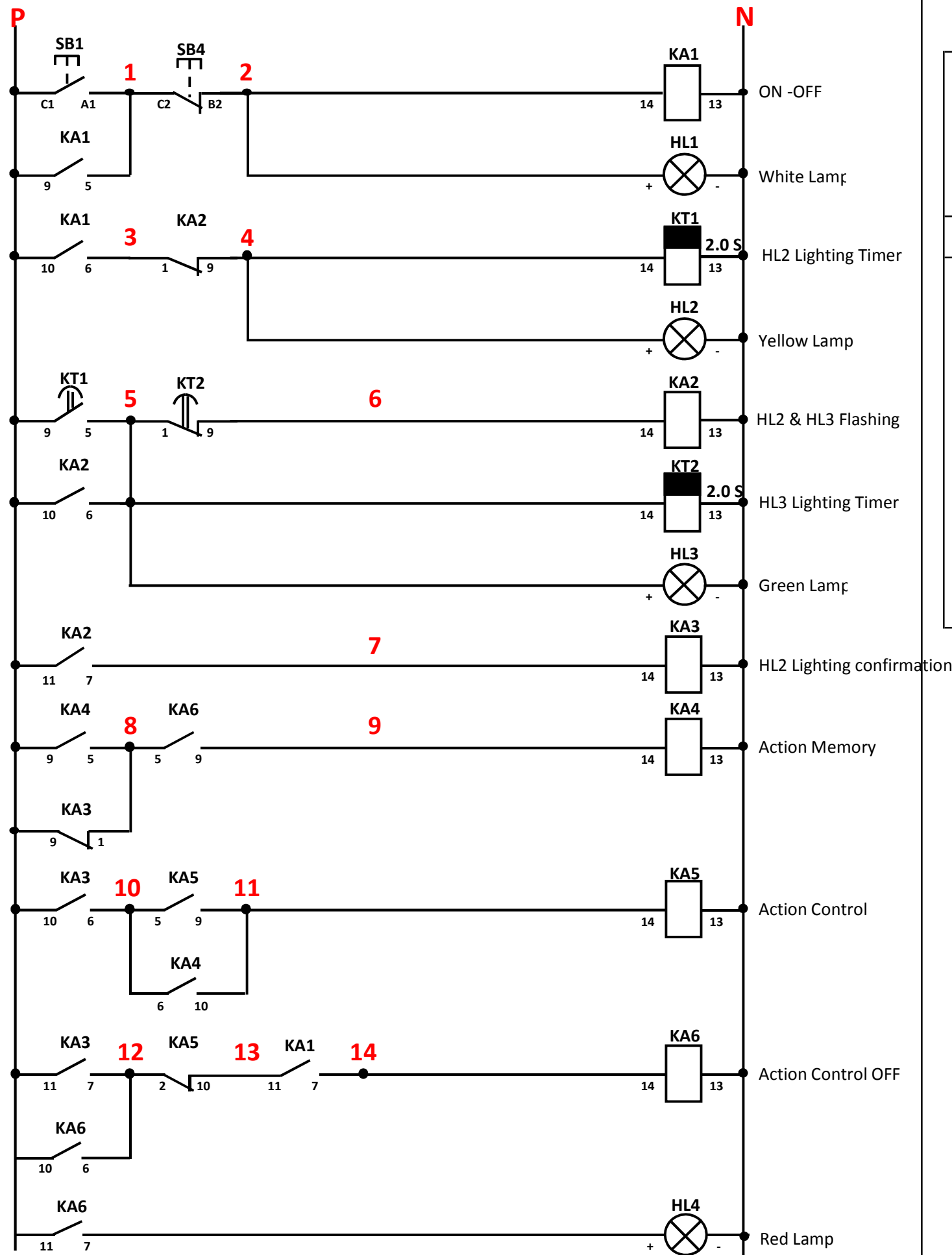


Control circuit Relay TMC_Ex_02



- ① When [SB1] is ON, [HL1] and [HL3] light up.
- ② [HL2] and [HL3] flash alternately. [HL4] uses the [HL3] lighting memory as a push-on/push-off circuit
- ③ When [SB4] is ON, [HL1] and [HL4] are extinguished. Also, if [HL3] is lit, it will turn off after the cycle is completed.

<Push ON, Push OFF Flicker circuit>

