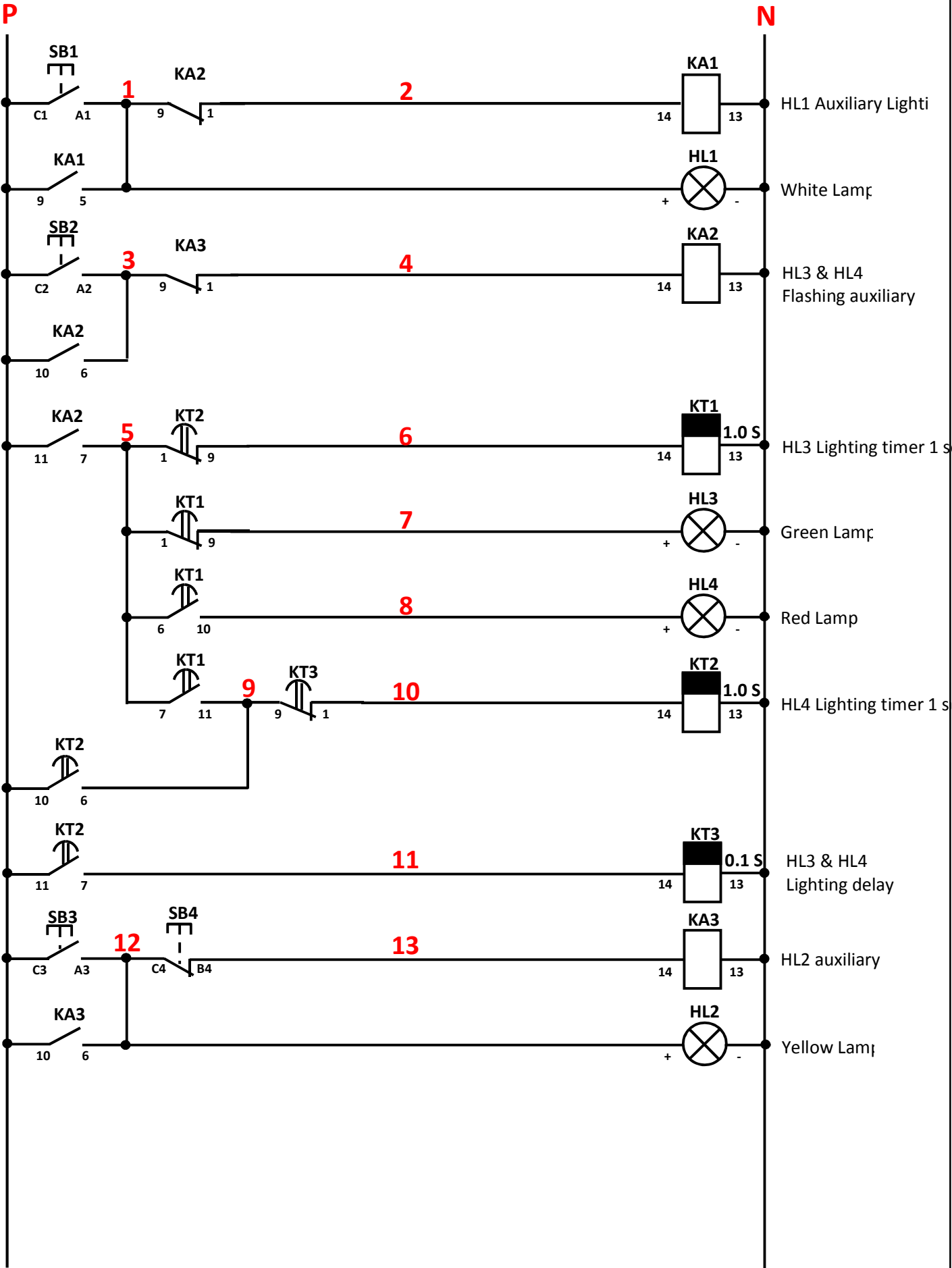


Control circuit Relay TMC_Ex_05



- ① When [SB1] is ON, [HL1] lights up.
- ② When [SB2] is ON, [HL1] is turned off. [HL3] and [HL4] flash alternately.
- ③ When [SB3] is ON, [HL3] and [HL4] are turned off. [HL2] lights up.
- ④ When [SB4] is ON, [HL2] is turned off.

<Sequential operation flicker>

