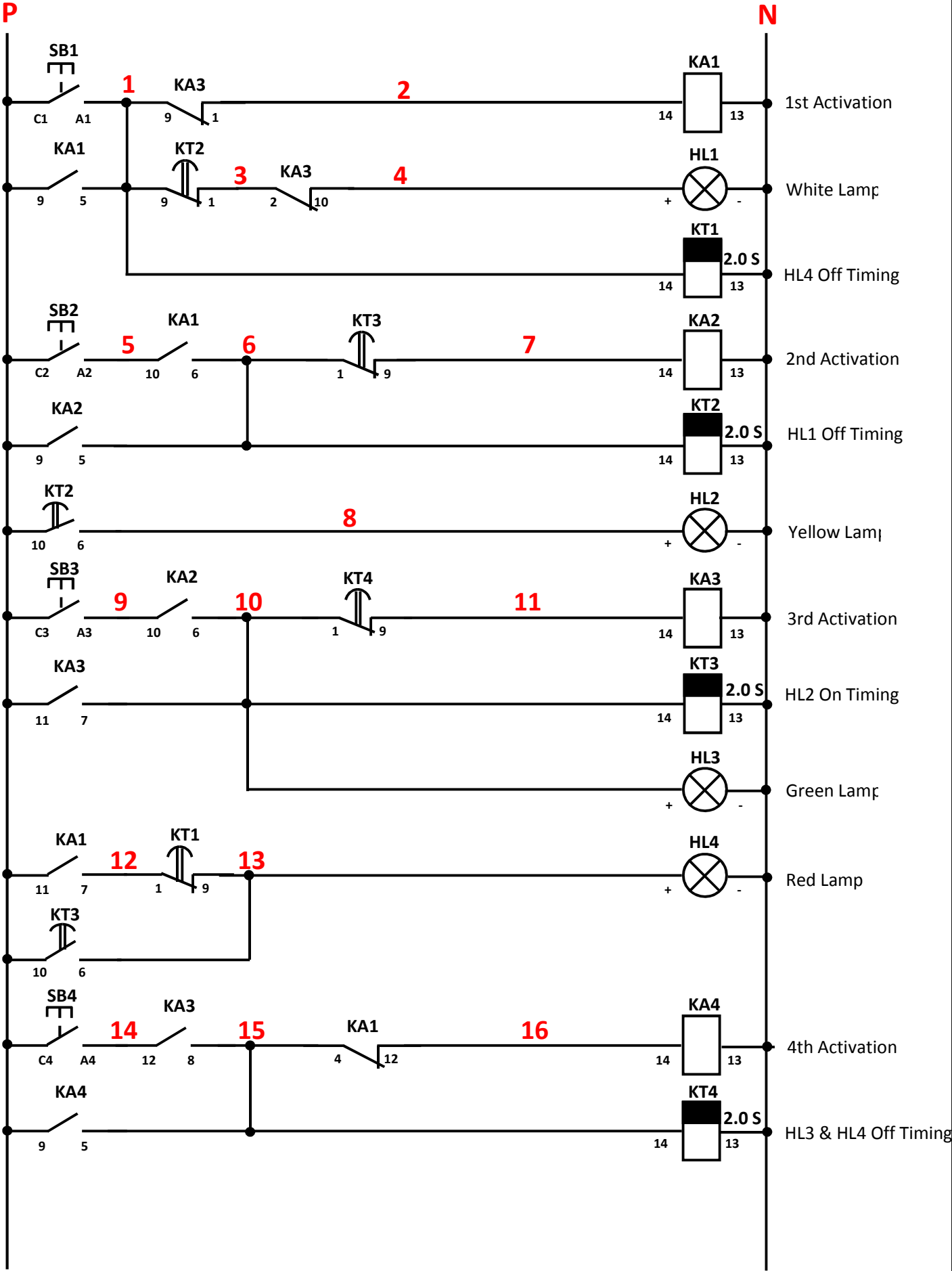


Control circuit Relay TMC_Ex_01



- ① When [SB1] is ON, [HL1] and [HL4] light up. Only [HL4] turns off after [KT1] time is up.
- ② After [SB2] is ON, [KT2] time is up, [HL1] is off, and [HL2] is on.
- ③ When [SB3] is ON, [HL3] lights up, and after [KT3] times up, [HL2] goes out, and [HL4] lights up.
- ④ After [SB4] is ON, [KT4] time up [HL3] and [HL4] go off.

<Normal movement>

①~④Repeat

